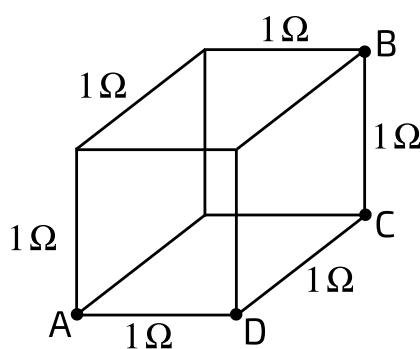


# Cube of Resistors

A Level



Imagine a cube of resistors, where each edge of the cube is a resistor of resistance  $1\ \Omega$ . In this question we will find the equivalent resistance between different vertices.



**Figure 1:** A cube of  $1\ \Omega$  resistors. Six of the twelve edges are labelled; all have the same resistance. Four of the vertices are labelled.

## Part A Resistance across main diagonal

What is the equivalent resistance between two vertices on the main diagonal, e.g. between points A and B in **Figure 1**? Give your answer to 3 s.f.

## Part B Resistance across diagonal of a face

What is the equivalent resistance between two vertices on the diagonal of a face, e.g. between points A and C in **Figure 1**? Give your answer to 3 s.f.

## Part C Resistance between adjacent vertices

What is the equivalent resistance between two adjacent vertices, e.g. between points A and D in **Figure 1**? Give your answer to 3 s.f.





## Power in a Potential Divider 10.8

A  $\mathcal{E} = 5.4 \text{ V}$  power supply (with  $r = 8.0 \, \Omega$ ) powers a  $50 \, \Omega$  phone. A voltmeter (with resistance  $200 \, \Omega$ ) is connected to measure  $V$ .

### Part A   Voltage $V$

How much voltage  $V$  is measured across the phone?

### Part B   Power delivered

Calculate the power delivered to the phone.



# Potential dividers with LEDs 8.1

Quantities:

$\varepsilon$  e.m.f. (V)

$V$  p.d. across fixed resistor (V)

$V_{\text{LED}}$  p.d. across LED (V)

$I$  current through circuit (A)

$R$  fixed resistor resistance ( $\Omega$ )

$E$  photon energy (J)

$\lambda$  wavelength of emitted light (m)

Equations:

$$V = IR \quad \varepsilon = V_{\text{LED}} + V \quad V_{\text{LED}} = \frac{E}{e} \quad E = \frac{hc}{\lambda}$$

Use the equations above to derive expressions for:

## Part A The resistance of the fixed resistor $R$

the resistance of the fixed resistor  $R$  in terms of the e.m.f.  $\varepsilon$ , the p.d. across the LED  $V_{\text{LED}}$  and the current  $I$ .

The following symbols may be useful:  $I$ ,  $R$ ,  $V_{\text{LED}}$ ,  $\varepsilon$


## Part B The resistance of the fixed resistor $R$ , using $\lambda$

the resistance of the fixed resistor  $R$  in terms of the e.m.f.  $\varepsilon$ , the wavelength of the LED  $\lambda$ , the current  $I$  and the physical constants  $h$ ,  $c$  and  $e$ .

The following symbols may be useful:  $I$ ,  $R$ ,  $c$ ,  $e$ ,  $\varepsilon$ ,  $h$ ,  $\lambda$

## Potential Dividers with LEDs 8.3

A blue LED produces light of wavelength  $480 \text{ nm}$ . It is powered using a  $9.00 \text{ V}$  battery using the circuit design shown below. Assume that there is no internal resistance in the power supply.

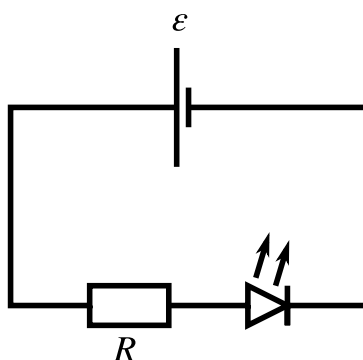

**Figure 1:** A circuit with a single cell in series with a resistor and an LED.

### Part A The p.d. across the LED

Calculate the p.d. across the LED.

---

### Part B The minimum value of $R$

Calculate the minimum value of  $R$  to ensure the current through the LED does not exceed  $50.0 \text{ mA}$ .

---

### Part C The resistance of the LED

Calculate the resistance of the LED.


---

# Transforming Resistors

A Level



The two resistor networks below can be called equivalent if they have the same electrical properties when viewed between any two of the terminals  $A$ ,  $B$  or  $C$ .  $R_a$ ,  $R_b$  and  $R_c$  can be given values based on the values of  $R_x$ ,  $R_y$  and  $R_z$  in order to make the two networks equivalent.

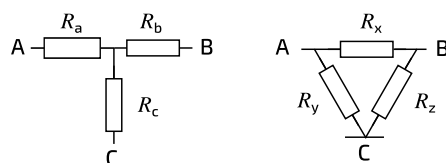


**Figure 1:** Two resistor networks.

## Part A Expression for $R_a$

If the two resistor networks of **Figure 1** are equivalent, find an expression for  $R_a$  in terms of  $R_x$ ,  $R_y$  and  $R_z$ .

The following symbols may be useful:  $R_a$ ,  $R_x$ ,  $R_y$ ,  $R_z$

## Part B A circuit

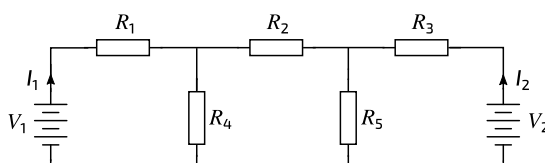

**Figure 2:** A circuit with two cells and five resistors.


Using the transformation and your result from Part A, or otherwise, work out the value of the current  $I_1$  in the circuit of **Figure 2**. You are given that  $R_1 = 1.0 \, \Omega$ ,  $R_2 = R_4 = R_5 = 3.0 \, \Omega$ ,  $R_3 = 2.0 \, \Omega$ ,  $V_1 = 22 \, \text{V}$  and  $V_2 = 11 \, \text{V}$ .

# Rambunctious Resistors

A Level



The circuit diagram below shows a combination of resistors with equivalent resistance  $R_{\text{eq}} = 37.0 \, \Omega$ .

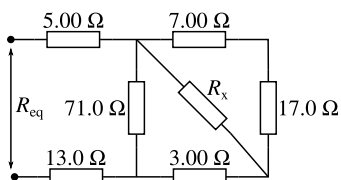

**Figure 1:** Circuit diagram showing how the resistors are arranged and the values of the resistances. The unknown resistor has resistance  $R_x$ .


What value of resistance  $R_x$  for the unknown resistor satisfies this value for the equivalent resistance?

# Non-linear I-V

GCSE A Level



The circuit below contains a metal oxide rod, represented by a dashed line. The potential difference (in volts) across the rod is given by  $V = 0.200I^2$  where  $I$  is the current (in amps) through the rod. This relationship is only valid for  $I > 0$ .

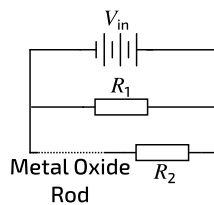

**Figure 1:** Circuit diagram showing how the rod, resistors and cell are connected to each other.

Given that  $R_1 = 3.00 \, \Omega$ ,  $R_2 = 2.00 \, \Omega$  and  $V_{in} = 6.00 \, \text{V}$  what is the total current drawn from the cell?

Adapted with permission from UCLES, A Level Physics, June 1961, Paper 3, Question 8

All materials on this site are licensed under the [Creative Commons license](#), unless stated otherwise.





## Current Division 9.4

---



I am going to connect two resistors in parallel to share a 13 A current so that 5.0 A flows through one resistor. The resistor with the larger resistance is a  $2.2\ \Omega$  resistor. Calculate the resistance of the other resistor.

---



Physics. *You work it out.*

[Home](#)   [Physics](#)   [Electricity](#)   [Resistors](#)   [Current Division 9.2](#)

## Current Division 9.2

---



A  $9.0\ \Omega$  resistor is connected in parallel with a  $81\ \Omega$  resistor. What fraction of the total current flows through the  $81\ \Omega$  resistor?

---

All materials on this site are licensed under the [Creative Commons license](#), unless stated otherwise.



## Power in a Potential Divider 10.2

---

Calculate the load power  $P$  for an  $\mathcal{E} = 240 \text{ V}$  generator with internal resistance  $2.5 \Omega$  when it is supplying  $4.2 \text{ A}$ .

---