

Circuits extension question

What is the power dissipated across the $50\ \Omega$ resistor?

