
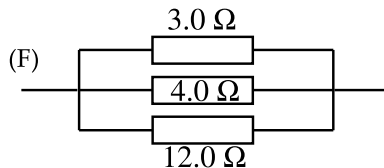
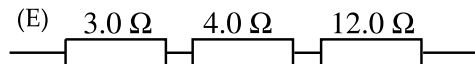
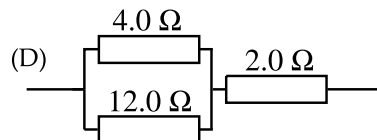
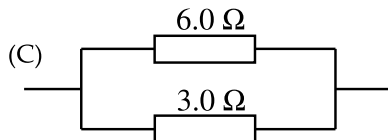
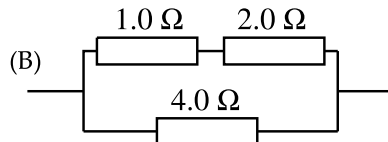


# C1 Combinations of Resistors

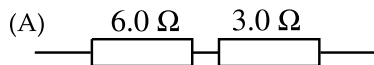

What is the resistance of labelled combination?

C1.1 a) A

b) B

C1.2 a) C

b) D

C1.3 a) E

b) F

## Resistivity

Complete the questions in the table:

Length /m	Wire thickness	Resistivity / $\Omega$ m	Resistance / $\Omega$
68	cross sectional area: $2.1 \times 10^{-6} \text{ m}^2$	$1.5 \times 10^{-8}$	C1.4
C1.5	cross sectional area: $0.50 \times 10^{-6} \text{ m}^2$	$4.9 \times 10^{-7}$	15
1.0	1.0 mm radius	$4.9 \times 10^{-7}$	C1.6
15000	1.0 cm diameter	$1.5 \times 10^{-7}$	C1.7

- C1.8 Conventional domestic 13 A sockets are connected with copper cables with a cross sectional area of  $2.5 \text{ mm}^2$ . Copper has a resistivity of  $1.5 \times 10^{-8} \Omega \text{ m}$ . What is the resistance of 20 m of cable?
- C1.9 A high voltage wire for transmission of electricity across the country is made of 10 aluminium wires (resistivity =  $2.5 \times 10^{-8} \Omega \text{ m}$ ) wound together with 15 copper wires (resistivity of  $1.5 \times 10^{-8} \Omega \text{ m}$ ). If all of the wires have a radius of 2.0 mm, calculate the overall resistance of 20 km of cable. (The aluminium is there to give strength to the cable.)