
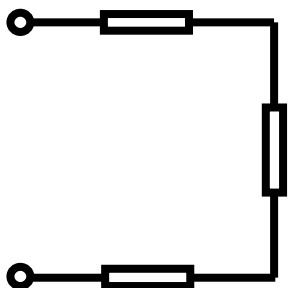



Combining resistors: extension question

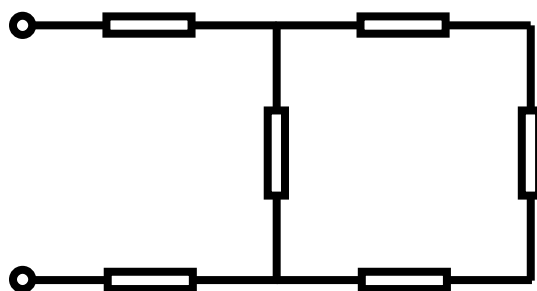


If each of the resistors in this network has a resistance R , the resistance of the network above is $3R$



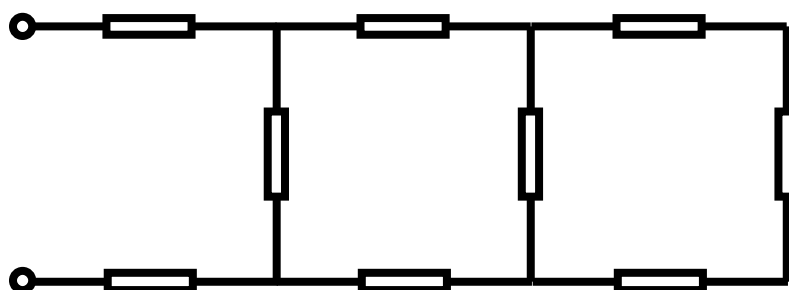If each of the resistors in this network has a resistance R , the resistance of the network above is $2R + \left(\frac{1}{R} + \frac{1}{3R}\right)^{-1}$



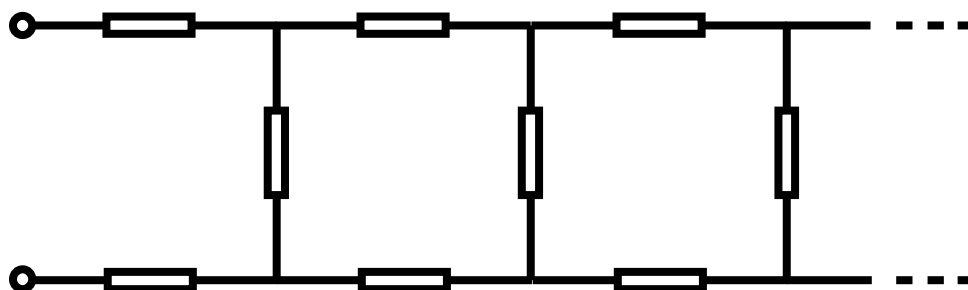If each of the resistors in this network has a resistance R , the resistance of the network above is $2R + \left(\frac{1}{R} + \frac{1}{2R + \left(\frac{1}{R} + \frac{1}{3R}\right)^{-1}}\right)^{-1}$



If the network of resistors repeats like this with an infinite number of additional branches;

- write an expression for the resistance of the network, Q , in terms of R ,
- calculate what the resistance would be if R was equal to $1\ \Omega$, and $2\ \Omega$.